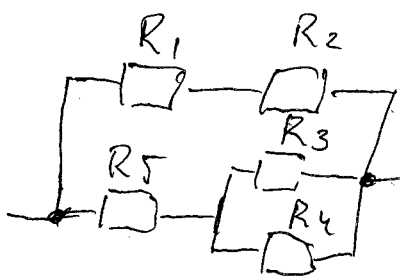


$$R_1 = 15 \text{ Ом} \quad R_2 = 15 \text{ Ом} \quad R_3 = 20 \text{ Ом} \quad R_4 = 10 \text{ Ом} \quad R_5 = 10 \text{ Ом}$$

$$I_{\text{дог}} = 1 \text{ А}$$



$$R' = R_1 + R_2 = 15 + 15 = 30 \text{ Ом}$$

$$2) R'' = R_3 \cdot R_4 / (R_3 + R_4) = 20 \cdot 10 / (20 + 10) = 6,6 \text{ Ом}$$

$$3) R''' = R_5 + R'' = 10 + 6,6 = 16,6 \text{ Ом}$$


$$R_{\text{дог}} = R' \cdot R''' / (R' + R''') = 30 \cdot 16,6 / (30 + 16,6) =$$

$$= 14,1 \text{ Ом}$$

на нагрузке резисторе

Ток через резистор
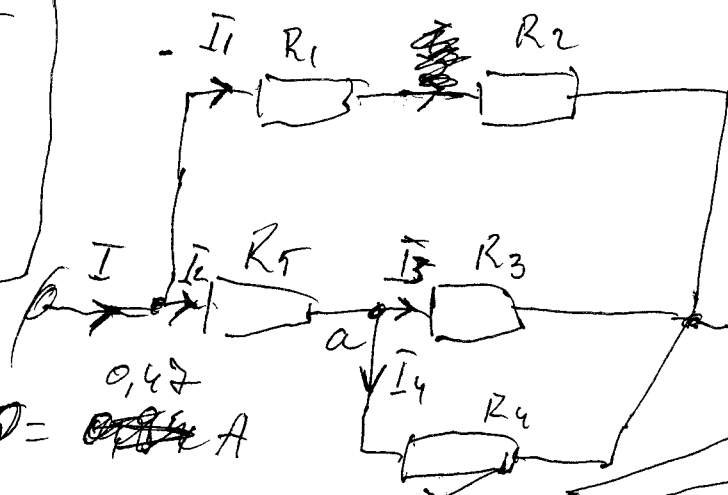
$$U = I \cdot R_{\text{дог}} = 1 \cdot 14,1 = 14,1 \text{ В}$$



$$I_{R1} = I_{R2} = I_1 = 0,47 \text{ А}$$

$$I_2 = I_3 + I_4 = 0,18 + 0,35 = 0,53 \text{ А}$$

$$I_{\text{дог}} = I_1 + I_2 = 0,53 + 0,47 = 1 \text{ А}$$

$$I_1 = U / R' = 14,1 / 30 = 0,47 \text{ А}$$

$$I_2 = U / R''' = 14,1 / 26,6 = 0,53 \text{ А}$$

$$U = I_2 \cdot R_5 = 10,6 \text{ В}$$

$$U_a = U_{\text{дог}} - U = 14,1 - 10,6 = 3,5 \text{ В}$$

$$I_3 = U_a / R_3 = 3,5 / 20 = 0,18 \text{ А}$$

$$I_4 = U_a / R_4 = 3,5 / 10 = 0,35 \text{ А}$$

Ответ: $R_{\text{дог}} = 14,1 \text{ Ом}$; Токи прох...

резисторов
 $R_1, R_2 = 0,47 \text{ А}$
 $R_5 = 0,53 \text{ А}$
 $R_3 = 0,18 \text{ А}$
 $R_4 = 0,35 \text{ А}$